



ISCAS 2021
Daegu, KOREA, MAY 22-28
IEEE International Symposium on Circuits and Systems



Ultra-Low Leakage ESD Protection Achieving 10.5 fA Leakage

Corentin Pochet, Haowei Jiang, and Drew A. Hall
University of California, San Diego

2021 IEEE International Symposium on Circuits and Systems
May 22-28, 2021 Virtual & Hybrid Conference




Need for Low-Leakage Interfaces

Many applications require input leakage below 50 fA:

- High-precision current front-ends
- High impedance sensor interfaces
- Ultra-low leakage voltage buffers

Achieving low leakage is challenging both at the PCB and chip level:

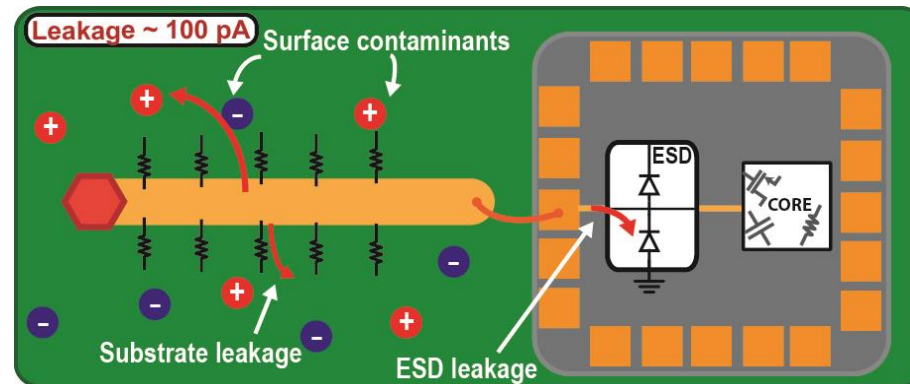- FR4 PCB substrate's resistivity is limited
- Surface contaminants are deposited on the PCB during fabrication and handling
- ESD protection diodes leakage is typically >100 fA




Techniques for Low-Leakage

Several techniques reduce the PCB leakage:

- Addition of guard traces surrounding the sensitive trace
- Removal of solder mask to avoid charge trapping
- Selection of a high resistivity substrate (e.g., Rogers 4003C)
- Washing and baking to remove surface contaminants

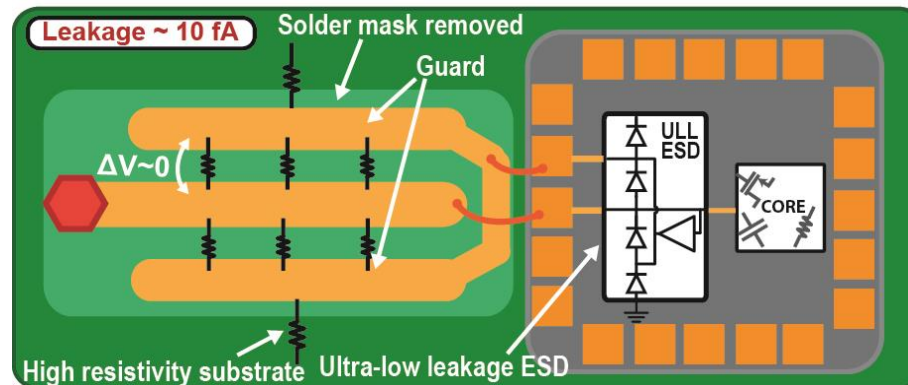PCB leakage reduced to $< 10 \text{ fA}$ → Need to reduce the ESD leakage




Typical solution for low leakage

Key idea: Reduce the voltage across the diodes to reduce leakage

Typical solution: Stack diodes to reduce ΔV

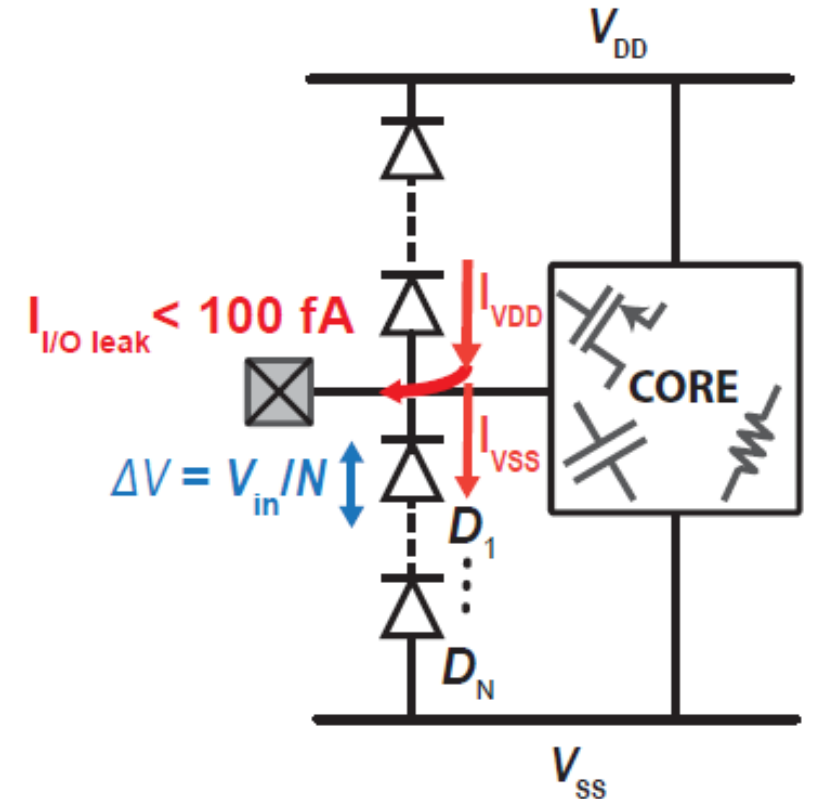Problems:

- Need large diode stack for low leakage
- Reduces the ESD resilience of the circuit




Proposed ESD Structure

Key idea: Reduce the voltage across the diodes to reduce leakage

Proposed Solution: Use a buffer to drive the voltage to $\sim 0V$

Buffer design guidelines:

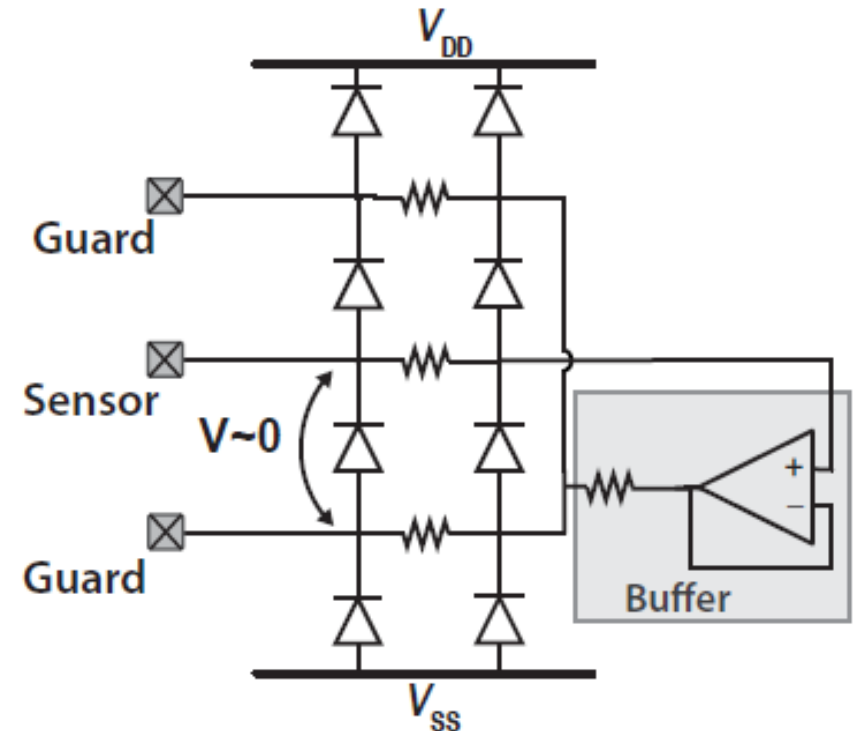- Thick oxide input devices
- Maximize input range
- Minimize offset through sizing and layout
- Minimize area & power




ESD resilience

ESD event : Extremely fast discharge (10s ns) of large current (1A)

ESD resilience guidelines:

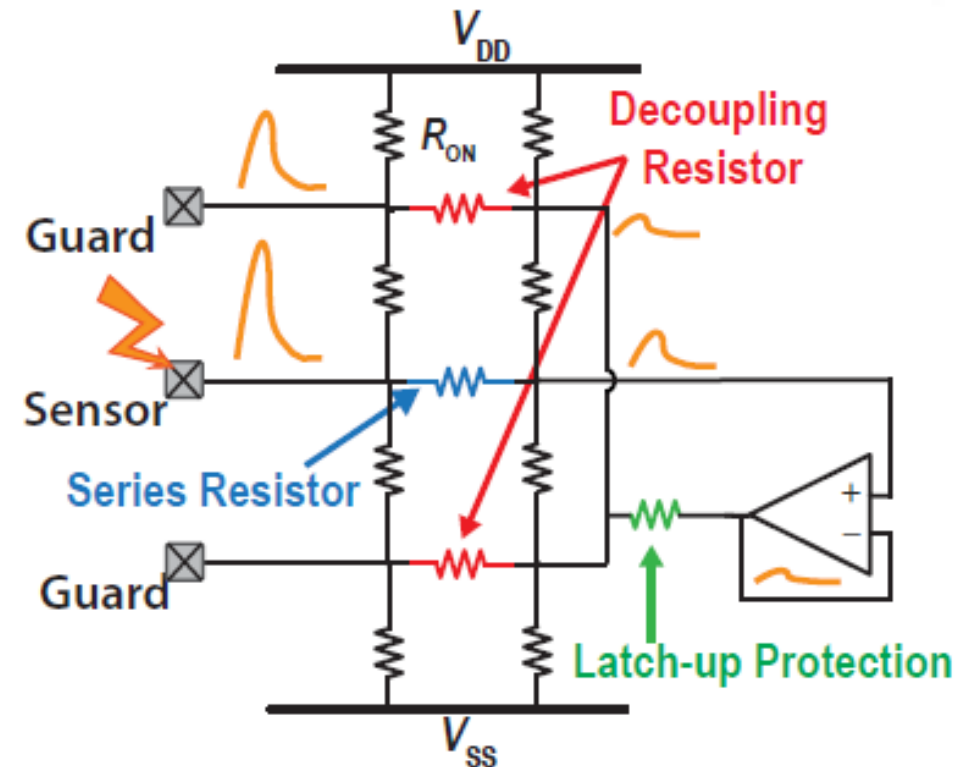- Minimize diode stacking
- Decoupling resistors between stages
- Latch-up protection resistor at the amplifier output




Test Chip and Measurement Setup

Test chip fabricated in **TSMC 180 nm** process

Three ESD structures implemented:

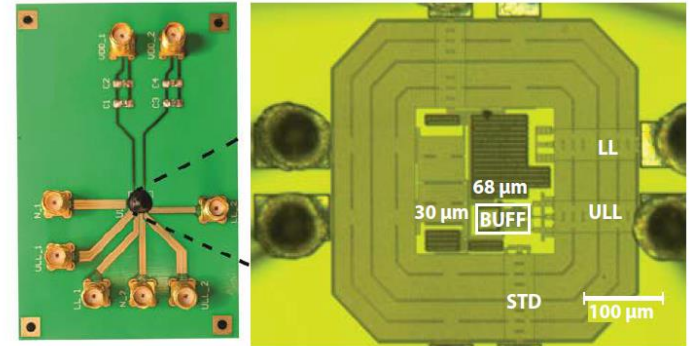- 1 diode standard (STD) structure
- 4 diodes stack low-leakage (LL) structure
- 2 diode stack with bootstrapping ultra-low-leakage (ULL) structure





Leakage measured using a source meter (**Keithley 6430**) in a temperature-controlled chamber (**TEQ 123H**)

- Bare PCBs exhibited a **~5 fA** leakage
- Chips bonded directly on board to avoid package leakage

Leakage Measurements

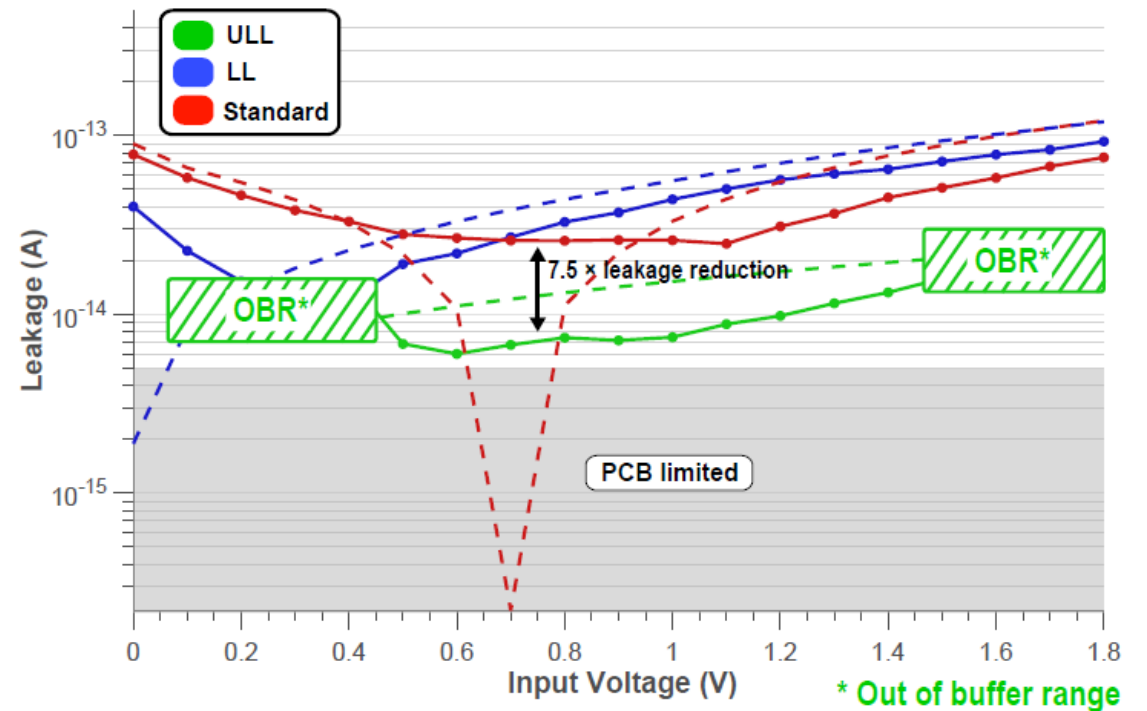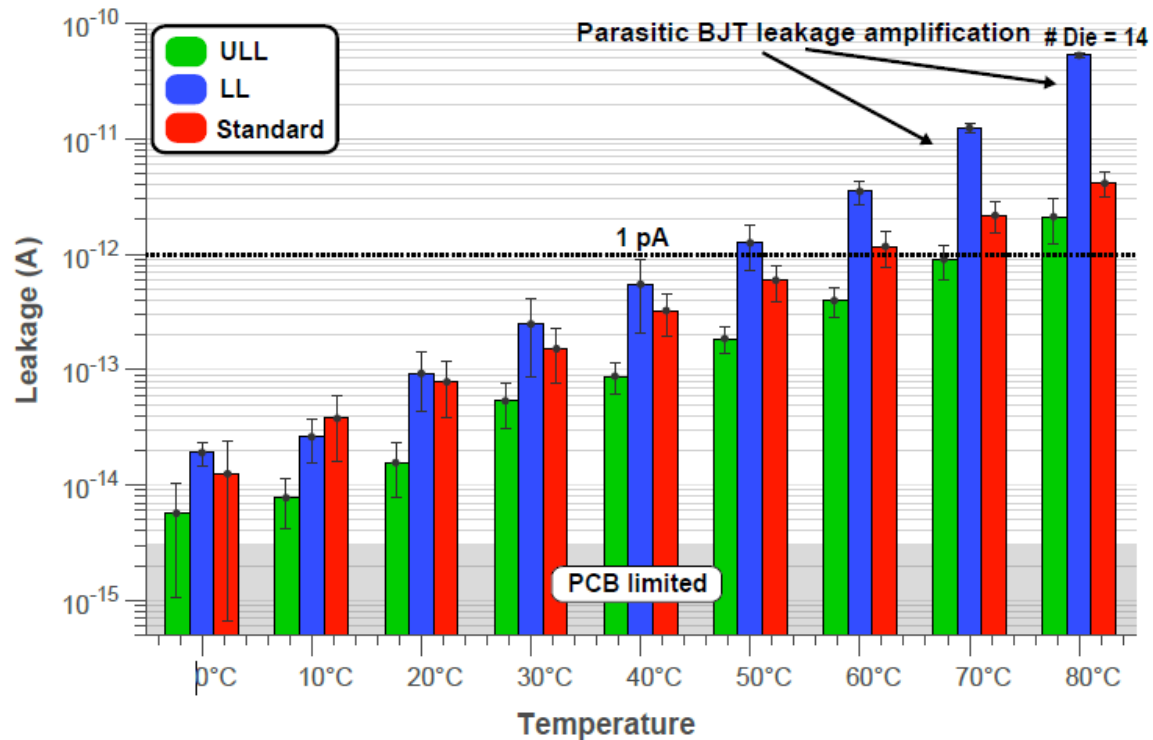Leakage measurements performed on 14 die across temperature and voltage



ULL structure improves the leakage performance by 7.5× and $I_{\max} = 10.5$ fA!

Conclusion

Some applications require extremely low leakage at the input interface that can't be achieved with standard PCB and ESD design.

Paper's contribution:

- Review of low leakage techniques for PCB and ESD
- Analysis and characterization of a diode bootstrapping technique for leakage reduction
- ESD resilience verified with Human-body model (HBM) ESD testing

Key results:

- **<10.5 fA** leakage in the input range of interest at room temperature
- High resilience to HBM ESD event (**5 kV**)
- Low power (**15 μ W**) and area (**0.002 mm²**) overhead

S1 - Standard ESD Structures

Typical ESD structures composed of diodes to the supply rails

- Shunt current in the event of an ESD event
- Large diodes to pass mA – A
- Multiple stages to improve protection (typically 2 for gate inputs)


The ESD diodes cause leakage

$$I_{\text{leak}} = I_{VDD} - I_{VSS} = I_s \left(e^{\frac{V_{\text{in}} - V_{DD}}{nV_t}} - e^{\frac{-V_{\text{in}}}{nV_t}} \right)$$

Intuitive solution is to stack multiple diodes

$$I_{\text{leak}} = I_{VDD} - I_{VSS} = I_s \left(e^{\frac{V_{\text{in}} - V_{DD}}{nV_t N}} - e^{\frac{-V_{\text{in}}}{nV_t N}} \right)$$

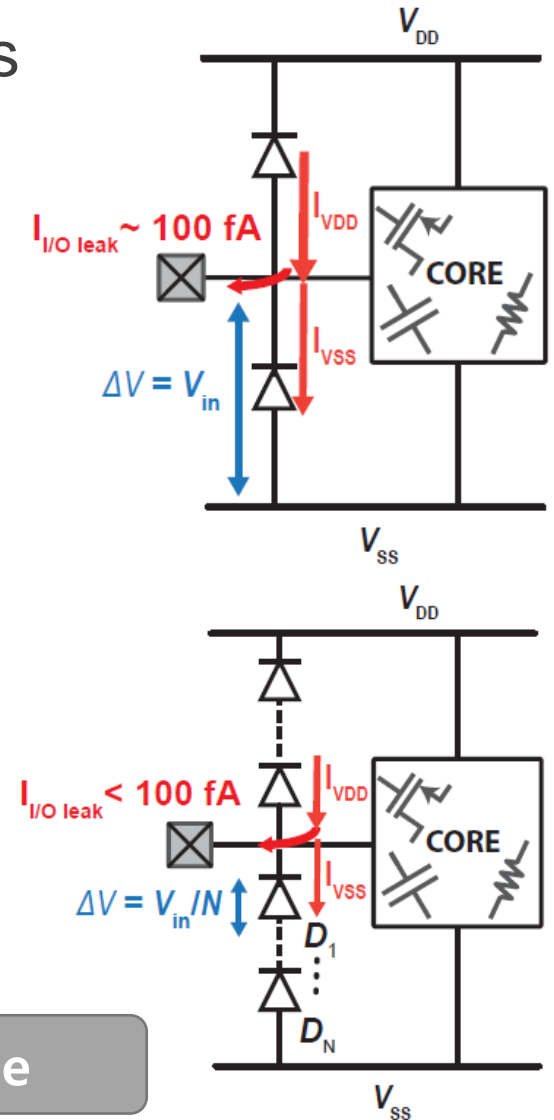Stacking reduces leakage but also ESD resilience



S2 - BJT leakage

Issue:

- Simulated and measured leakage deviates significantly.
- Leakage much worse at high temperature

Cause:

- Leakage limited by the parasitic BJTs formed with the substrate

Solution

- Effect could be reduced by using double N-well diodes with well tied to supplies

